

# EE281 - Phasors & Impedances

Dr. M. Mert ANKARALI

# Phasors & Sinusoidal Steady-State Analysis

- **Goal:** Perform only sinusoidal steady-state analysis
  - De we need to derive the ODE “first”

Time Domain

Phasor Domain

$$v(t) = A \cos(\omega t + \phi) \rightarrow V(j\omega) = Ae^{j\phi} = A\angle\phi$$

# Phasors & Sinusoidal Steady-State Analysis

- **Goal:** Perform only sinusoidal steady-state analysis
  - No need to find ODE “first”
- **Method:** Phasor notation & the concept of impedance

Time Domain

Phasor Domain

$$v(t) = A \cos(\omega t + \phi) \rightarrow V(j\omega) = Ae^{j\phi} = A\angle\phi$$

# Impedance

## Resistance: Time & Phase Domain

$$V(t) = R \cdot I(t)$$

$$V(j\omega) = R \cdot I(j\omega)$$

# Impedance

## Resistance: Time & Phase Domain

$$V(t) = R \cdot I(t)$$

$$V(j\omega) = R \cdot I(j\omega)$$

## Impedance in Phasor Domain

$$V(j\omega) = Z(j\omega) \cdot I(j\omega)$$

# Impedance

Time

Phasor

Impedance

**Resistor**

$$V(t) = R \cdot I(t) \implies V(j\omega) = R \cdot I(j\omega) \implies Z_R(j\omega) = R$$

**Capacitor**

**Inductor**

# Impedance

Time

Phasor

Impedance

**Resistor**

$$V(t) = R \cdot I(t) \implies V(j\omega) = R \cdot I(j\omega) \implies Z_R(j\omega) = R$$

**Capacitor**

$$C \frac{dV(t)}{dt} = I(t) \implies V(j\omega) = \frac{1}{j\omega C} I(j\omega) \implies Z_C(j\omega) = \frac{1}{j\omega C}$$

**Inductor**

# Impedance

Time

Phasor

Impedance

**Resistor**

$$V(t) = R \cdot I(t) \implies V(j\omega) = R \cdot I(j\omega) \implies Z_R(j\omega) = R$$

**Capacitor**

$$C \frac{dV(t)}{dt} = I(t) \implies V(j\omega) = \frac{1}{j\omega C} I(j\omega) \implies Z_C(j\omega) = \frac{1}{j\omega C}$$


**Inductor**


$$V(t) = L \frac{dI(t)}{dt} \implies V(j\omega) = j\omega L \cdot I(j\omega) \implies Z_L(j\omega) = j\omega L$$



Let  $R = 1\ \Omega$ ,  $C = 1\ \text{F}$

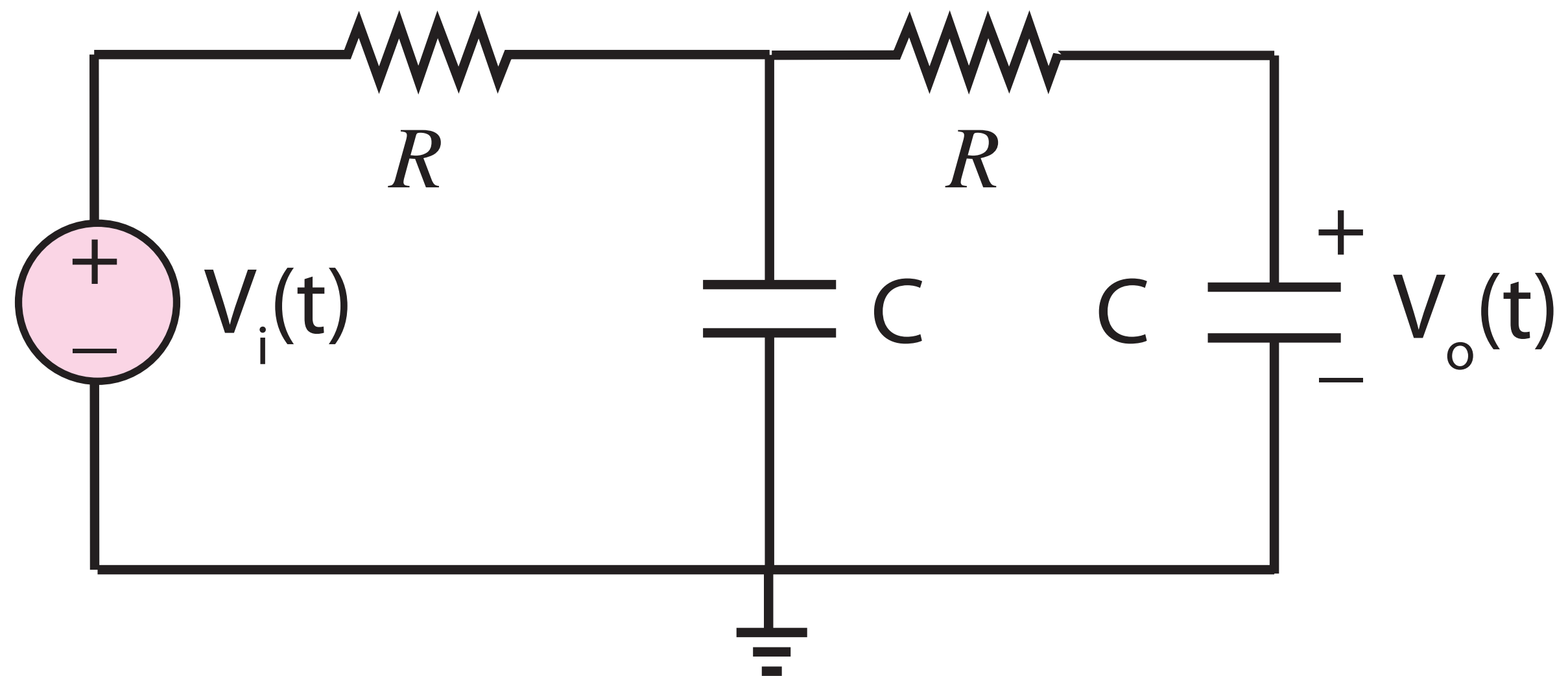$V_i(t) = \cos(\omega t)$  for  $\omega = 1.0\ \text{rad/s}$



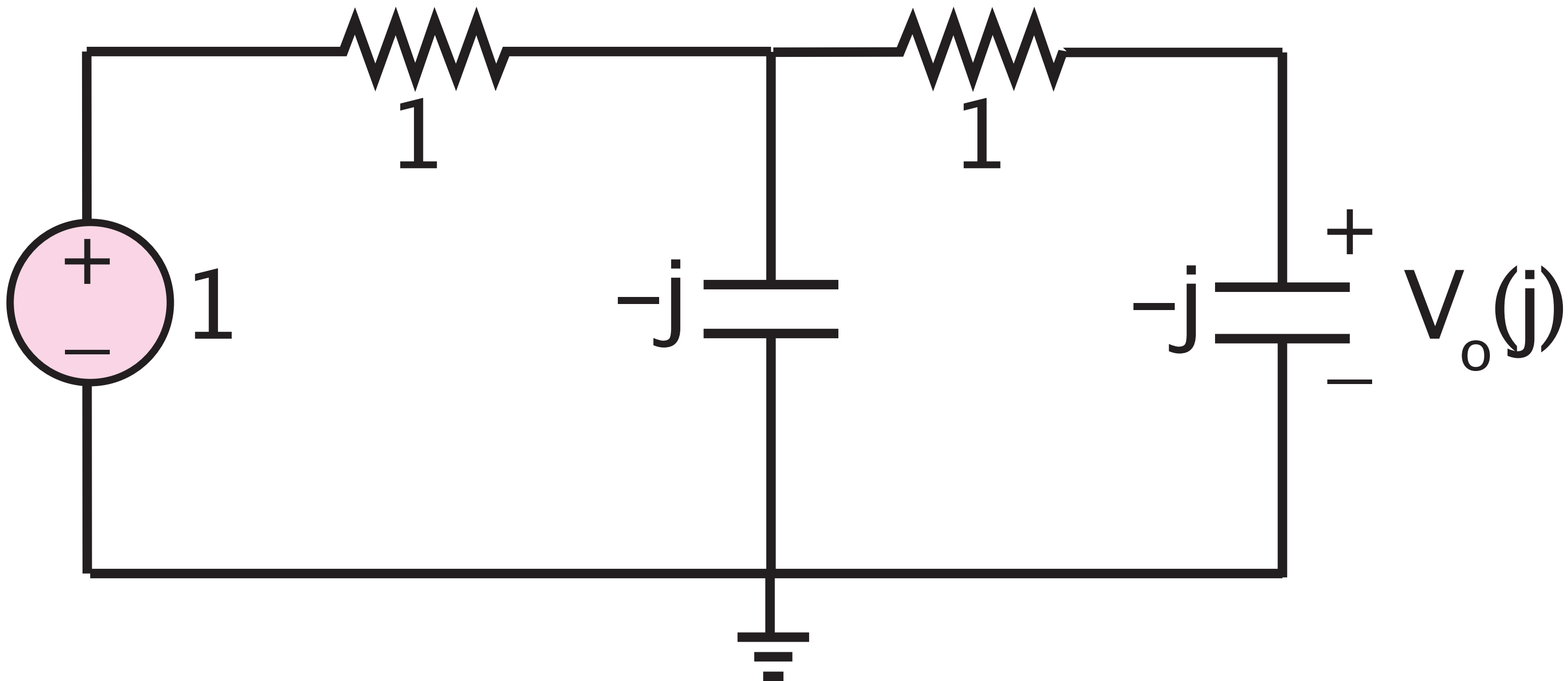


$$(V_a - 1) + \frac{V_a}{-j} + \frac{V_a}{1-j} = 0$$

$$V_a = \frac{2/3}{1+j}$$

$$V_o = \frac{V_a}{1-j} \cdot j = \frac{2/3}{1+j} \frac{-j}{1-j}$$

$$V_o = \frac{-j}{3} = \frac{1}{3} \angle -\frac{\pi}{2}$$

$$V_o(t) = \frac{1}{3} \cos(t - \pi/2)$$

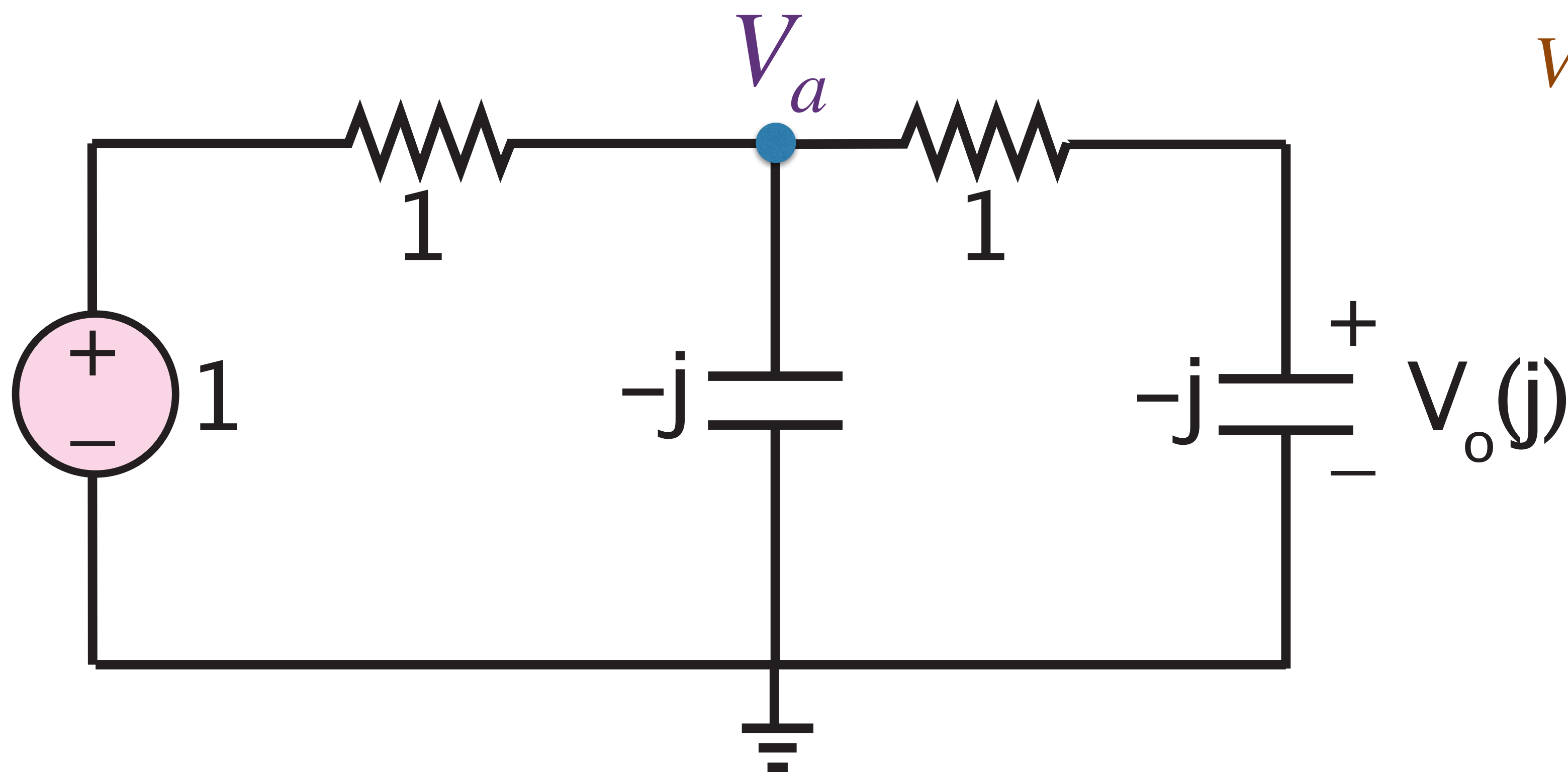

Let  $v_i(t) = \cos(10^3 t)$

