

CENG-232

Logic Design

Lecture 6


Sequential Circuit Design

Spring 2015 - Uluç Saranlı
saranli@ceng.metu.edu.tr

Acknowledgment: Most of the following slides are adapted from Prof. Kale's slides at UIUC, USA.

Sequential Circuit Design

 - ▶ In sequential circuit design, we turn some description into a working circuit.
 - ▶ We first make a state table or diagram to express the computation.
 - ▶ Then we can turn that table or diagram into a sequential circuit.



Sequence Recognizers

- ▶ A sequence recognizer is a special kind of sequential circuit that looks for a special bit pattern in some input.
- ▶ The recognizer circuit has only one input, X.
 - ▶ One bit of input is supplied on every clock cycle. For example, it would take 20 cycles to scan a 20-bit input.
 - ▶ This is an easy way to permit arbitrarily long input sequences.
- ▶ There is one output, Z, which is 1 when the desired pattern is found.
- ▶ Our example will detect the bit pattern “1001”:

Input:	1 1 1 0 0 1 1 0 1 0 0 1 0 0 1 1 0 ...
Output:	0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 0 ...



Sequence Recognizers (Cont'd.)

Inputs: 1 1 1 0 0 1 1 0 1 0 0 1 0 0 1 1 0 ...


Outputs: 0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 0 ...

- ▶ This requires a sequential circuit because the circuit has to “remember” the inputs from previous clock cycles, in order to determine whether or not a match was found.
- ▶ Here, one input and one output bit appear every clock cycle.
- ▶ Note that overlapping bit patterns are also detected.



A basic state diagram

 
- ▶ What state do we need for the sequence recognizer?
 - ▶ We have to “remember” inputs from previous clock cycles.
 - ▶ For example, if the previous three inputs were 100 and the current input is 1, then the output should be 1.
 - ▶ In general, we will have to remember occurrences of parts of the desired pattern - in this case, 1, 10, and 100.
- ▶ We'll start with a basic state diagram:



State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.

Overlapping pattern occurrences

 
- ▶ What happens if we're in state D (the last three inputs were 100), and the current input is 1?
 - ▶ The output should be a 1, because we've found the desired pattern.
 - ▶ But this last 1 could also be the start of another occurrence of the pattern! For example, 1001001 contains two occurrences of 1001.
 - ▶ To detect overlapping occurrences of the pattern, the next state should be B.



State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.


Filling in the other arrows

 - ▶ Remember that we need two outgoing arrows for each node, to account for the possibilities of $X=0$ and $X=1$.
- ▶ The remaining arrows are shown in blue. They also allow for the correct detection of overlapping occurrences of 1001.




State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.

Finally, making the state table

 

 Remember how the state diagram arrows correspond to rows of the state table:



Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

Sequential Circuit Design Procedure

- ▶ Step 1:

Make a state table based on the problem statement. The table should show the present states, inputs, next states and outputs. (It may be easier to find a state diagram first, and then convert that to a table.)

- ▶ Step 2:

Assign binary codes to the states in the state table, if you haven't already. If you have n states, your binary codes will have at least $\lceil \log_2 n \rceil$ digits, and your circuit will have at least $\lceil \log_2 n \rceil$ flip-flops.



Sequential circuit design procedure

- ▶ Step 3:

For each flip-flop and each row of your state table, find the flip-flop input values that are needed to generate the next state from the present state. You can use flip-flop excitation tables here.

- ▶ Step 4:

Find simplified equations for the flip-flop inputs and the outputs.

- ▶ Step 5:


Build the circuit!



Step 2: Assigning binary codes

- ▶ We have four states ABCD, so we need at least two flip-flops Q_1Q_0 .
- ▶ The easiest thing to do is represent state A with $Q_1Q_0 = 00$, B with 01, C with 10, and D with 11 (intuitive).
- ▶ The state assignment can have a big impact on circuit complexity, but we won't worry about that too much in this class.

Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

 

Present State		Input X	Next State		Output Z
Q_1	Q_0		Q_1	Q_0	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Step 3: Finding flip-flop inputs

- ▶ Next we have to figure out how to actually make the flip-flops change from their present state into the desired next state.
- ▶ This depends on what kind of flip-flops you use!
- ▶ We'll use two JKs. For each flip-flop Q_i , look at its present and next states, and determine what the inputs J_i and K_i should be in order to make that state change.

Present State		Input X	Next State		Flip flop inputs				Output Z
Q_1	Q_0		Q_1	Q_0	J_1	K_1	J_0	K_0	
0	0	0	0	0					0
0	0	1	0	1					0
0	1	0	1	0					0
0	1	1	0	1					0
1	0	0	1	1					0
1	0	1	0	1					0
1	1	0	0	0					0
1	1	1	0	1					1

Finding JK flip-flop input values

- ▶ For JK flip-flops, this is a little tricky. Recall the characteristic table:

J	K	$Q(t+1)$	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

- ▶ If the present state of a JK flip-flop is 0 and we want the next state to be 1, then we have two choices for the JK inputs:
 - ▶ We can use $JK=10$, to explicitly set the flip-flop's next state to 1.
 - ▶ We can also use $JK=11$, to complement the current state 0.
- ▶ So to change from 0 to 1, we must set $J=1$, but K could be either 0 or 1.
- ▶ Similarly, the other possible state transitions can all be done in two different ways as well.



JK excitation table

- ▶ An excitation table shows what flip-flop inputs are required in order to make a desired state change.


Q(t)	Q(t+1)	J	K	Operation
0	0	0	x	No change/reset
0	1	1	x	Set/complement
1	0	x	1	Reset/complement
1	1	x	0	No change/set

- ▶ This is the same information that's given in the characteristic table, but presented “backwards.”


J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement




Excitation Tables for all flip-flops

 

Q(t)	Q(t+1)	D	Operation
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

 

Q(t)	Q(t+1)	J	K	Operation
0	0	0	x	No change/reset
0	1	1	x	Set/complement
1	0	x	1	Reset/complement
1	1	x	0	No change/set

 

Q(t)	Q(t+1)	T	Operation
0	0	0	No change
0	1	1	Complement
1	0	1	Complement
1	1	0	No change



Back to the Example

- We can now use the JK excitation table on the right to find the correct values for each flip-flop's inputs, based on its present and next states.

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Present State		Input X	Next State		Flip flop inputs				Output Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1

Step 4: Find FF in/out equations

- ▶ Now you can make K-maps and find equations for each of the four flip-flop inputs, as well as for the output Z.
- ▶ These equations are in terms of the present state and the inputs.
- ▶ The advantage of using JK flip-flops is that there are many don't care conditions, which can result in simpler equations.

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

Present State		Input X	Next State		Flip flop inputs				Output
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	Z
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1


Step 5: Build the Circuit

- ▶ Lastly, we use these simplified equations to build the completed circuit.

$$J_1 = X' Q_0$$
$$K_1 = X + Q_0$$


$$J_0 = X + Q_1$$
$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

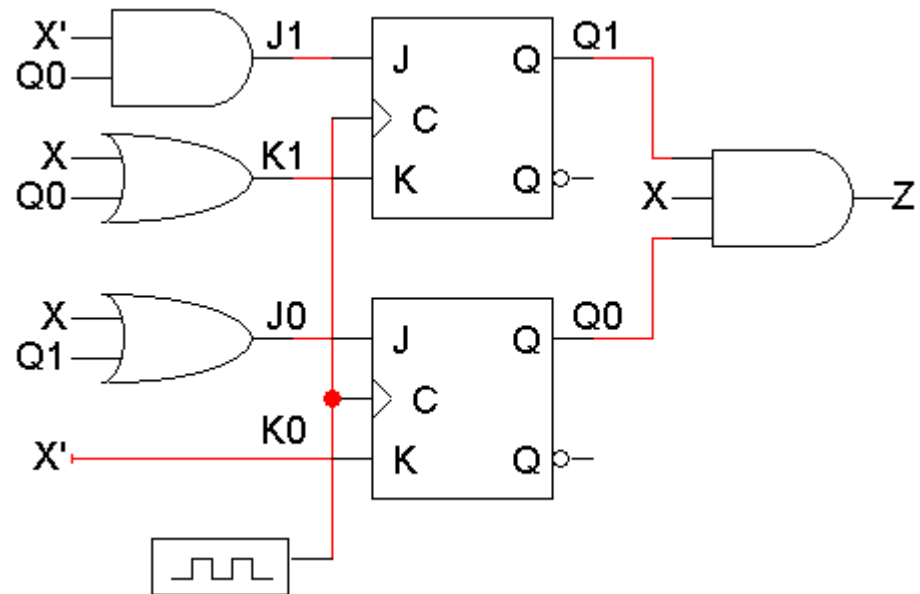

Timing Diagram

- ▶ Here is one example timing diagram for our sequence detector.
 - ▶ The flip-flops Q_1Q_0 start in the initial state, 00.
 - ▶ On the first three positive clock edges, X is 1, 0, and 0. These inputs cause Q_1Q_0 to change, so after the third edge $Q_1Q_0 = 11$.
 - ▶ Then when $X=1$, Z becomes 1 also, meaning that 1001 was found.
- ▶ The output Z does not have to change at positive clock edges. Instead, it may change whenever X changes, since $Z = Q_1Q_0X$.

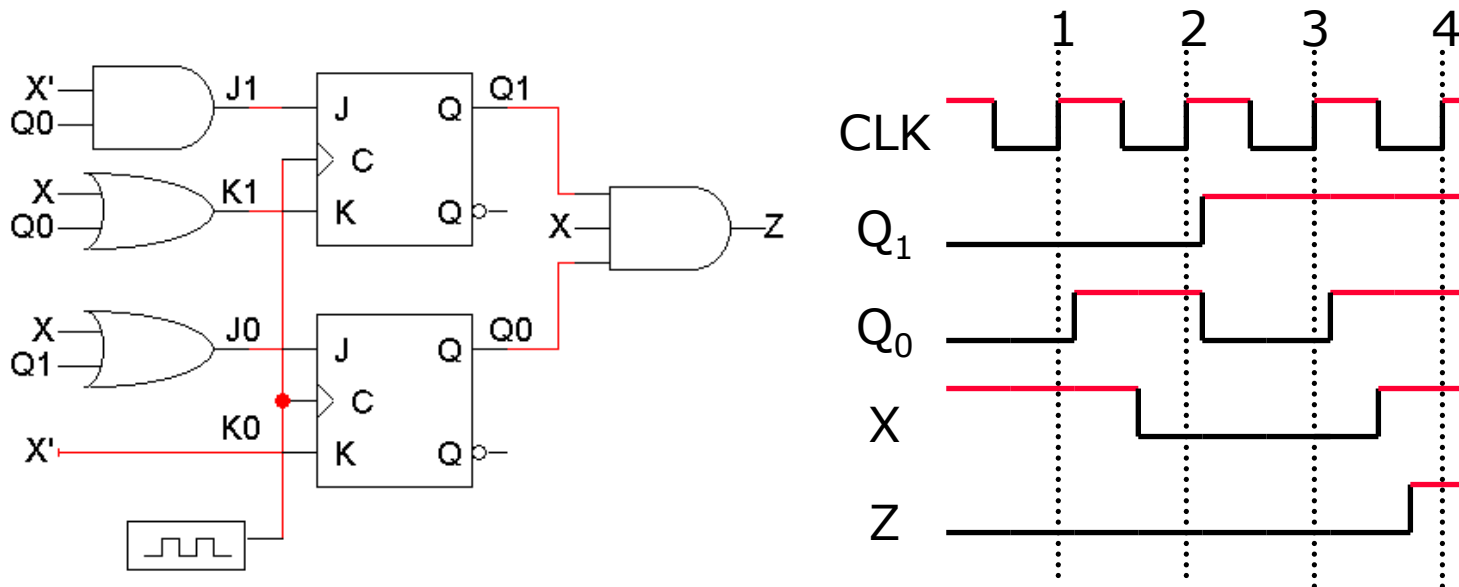

Using D flip-flops

- ▶ What if you want to build the circuit using D flip-flops instead?
- ▶ We already have the state table and state assignments, so we can just start from Step 3, finding the flip-flop input values.
- ▶ D flip-flops have only one input, so our table only needs two columns for D1 and D0.

Present State		Input X	Next State		Flip-flop inputs		Output Z
Q ₁	Q ₀		Q ₁	Q ₀	D ₁	D ₀	
0	0	0	0	0			0
0	0	1	0	1			0
0	1	0	1	0			0
0	1	1	0	1			0
1	0	0	1	1			0
1	0	1	0	1			0
1	1	0	0	0			0
1	1	1	0	1			1



D flip-flop input values (Step 3)

- ▶ The D excitation table is pretty boring; set the D input to whatever the next state should be.

Q(t)	Q(t+1)	D	Operation
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

- ▶ You don't even need to show separate columns for D1 and D0; you can just use the Next State columns.

Present State		Input X	Next State		Flip flop inputs		Output Z
Q ₁	Q ₀		Q ₁	Q ₀	D ₁	D ₀	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1

The same

Finding Equations (Step 4)

- ▶ You can do K-maps again, to find:

$$D1 = Q1 Q0' X' + Q1' Q0 X'$$


$$D0 = X + Q1 Q0'$$

$$Z = Q1 Q0 X$$


Present State		Input X	Next State		Flip flop inputs		Output Z
Q ₁	Q ₀		Q ₁	Q ₀	D ₁	D ₀	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1




Building the Circuit (Step 5)

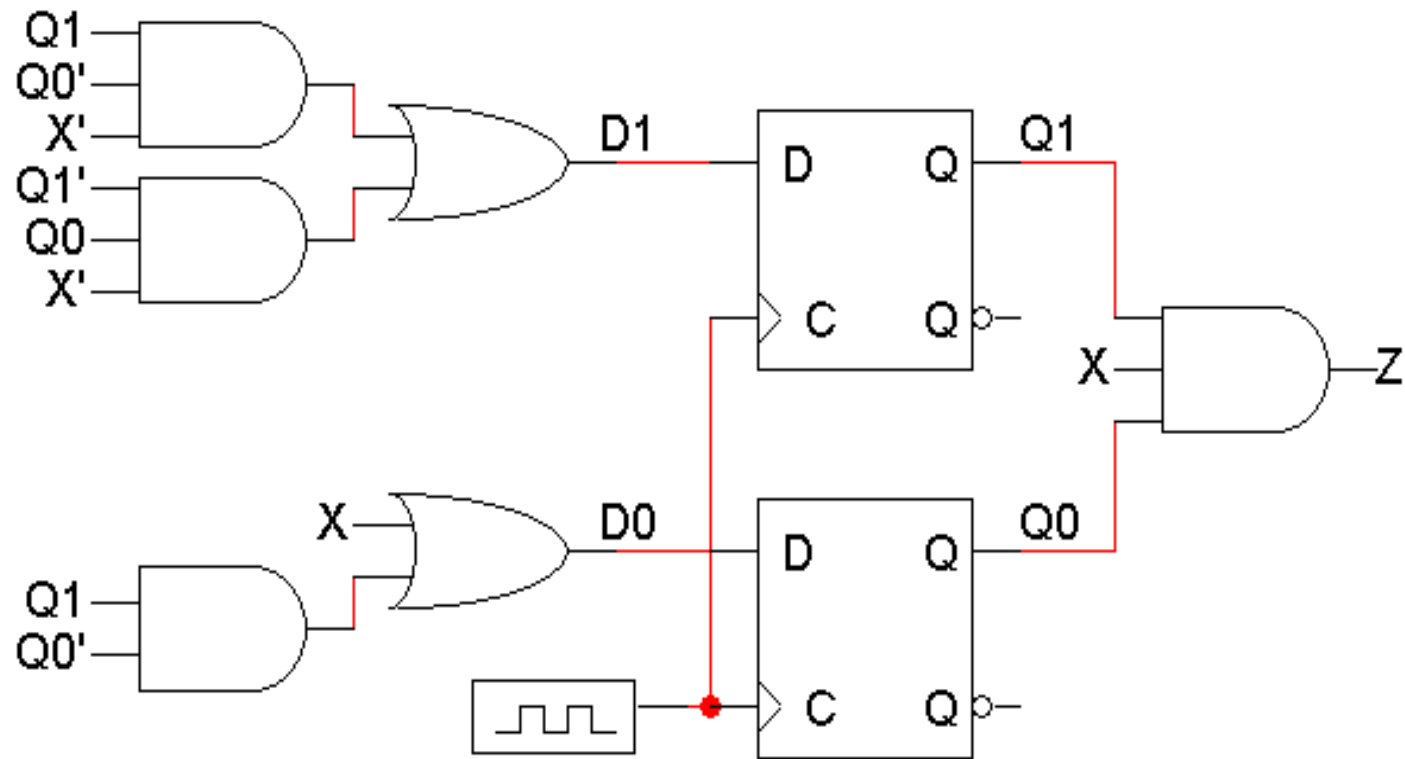


Flip-flop comparison

 

 JK flip-flops are good because there are many don't care values in the flip-flop inputs, which can lead to a simpler circuit.



 D flip-flops have the advantage that you don't have to set up flip-flop inputs at all, since $Q(t+1) = D$. However, the D input equations are usually more complex than JK input equations



In practice, D flip-flops are used more often.

There is only one input for each flip-flop, not two.

There are no excitation tables to worry about.

D flip-flops can be implemented with slightly less hardware than JK flip-flops.



Summary

- ▶ The basic sequential circuit design procedure:
 - ▶ Make a state table and, if desired, a state diagram. This step is usually the hardest.
 - ▶ Assign binary codes to the states if you didn't already.
 - ▶ Unused states can be treated as don't care conditions.
 - ▶ Use the present states, next states, and flip-flop excitation tables to find the flip-flop input values.
 - ▶ Write simplified equations for the flip-flop inputs and outputs and build the circuit.
- ▶ Next; how do we minimize the states to be used?
 - ▶ Do we need that?



Work ...

- ▶ Design a sequential circuit that detects 01 patterns coming through an input line X. The circuit's output Z should be set 1 when a 01 pattern occurs and to 0 otherwise.

X	01110001000010
Z	01000001000010

- ▶ Draw the state diagram of the circuit
- ▶ Derive the state table
- ▶ Implement using D-FF's
 - ▶ Extend the state table for D-FF inputs
 - ▶ Derive the expressions for D-FF inputs
 - ▶ Draw the full circuit



State Reduction and Assignment

- ▶ Goal: Reduce the number of states while keeping the external input-output requirements.
- ▶ 2^m states need m flip-flops, so reducing the states may reduce flip-flops.
- ▶ If two states are equal, one can be removed but what are “equal states”?
 - ▶ State Equivalence



State Reduction Example

As an example consider the input sequence below:

“010101110100” applied and start from state a.

State	a	a	b	c	d	e	f	f	g	f	g	a
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	

 


Fig. 5-22 State Diagram

State Reduction Example

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

 


Fig. 5-22 State Diagram

State Reduction Example

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

States e and g are equal since for each member of the set of inputs, they give the same output and send the circuit either to the same state or an equivalent state.

 


Fig. 5-22 State Diagram

State Reduction Example

<i>Present State</i>	<i>Next State</i>		<i>Output</i>	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g e	f	0	1
g	a	f	0	1

*Table and state diagram after the first reduction:
state g is removed and replaced by state e.*



State Reduction Example

<i>Present State</i>	<i>Next State</i>		<i>Output</i>	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1
g	a	f	0	1

Table and state diagram after the first reduction: g is removed and replaced by state e.

However, we now have NEW equal states: d and f



State Reduction Example

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1
f	e	f	0	1
g	a	f	0	1

 


Fig. 5-23 Reduced State Diagram

Table and state diagram after the second reduction: f is removed and replaced by state d.

If we apply the same input sequence:

State	a	a	b	c	d	e	d	d	e	d	e	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

