

# EE281 EXPERIMENT 4

Göktuğ Ekinici  
2380343


28th of November 2020(Took 6 Hours)

## 1 Preliminary Work

### 1.1 Question 1


a.  $V_3 = V_2$

$$V_{in} = V_{out}$$

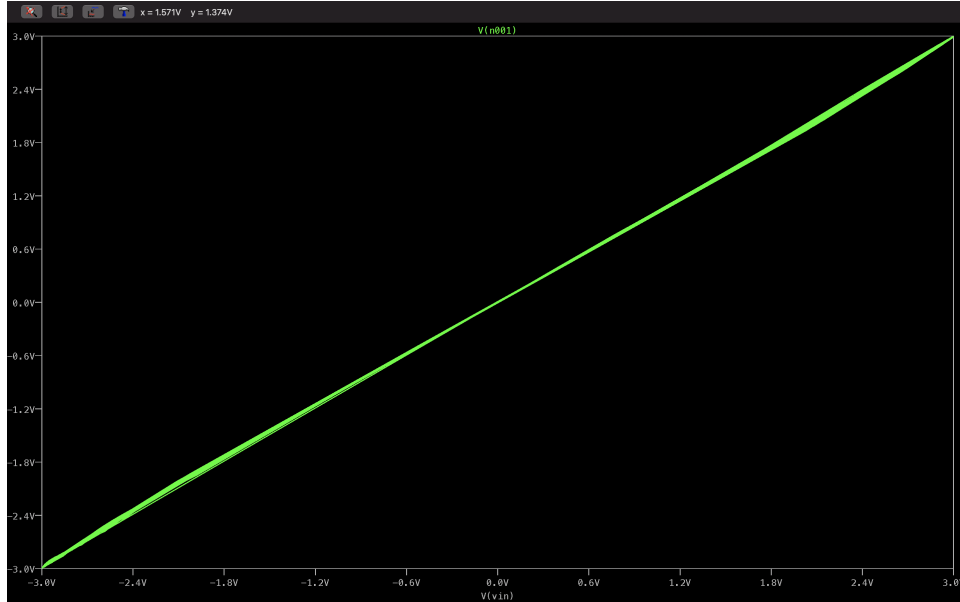

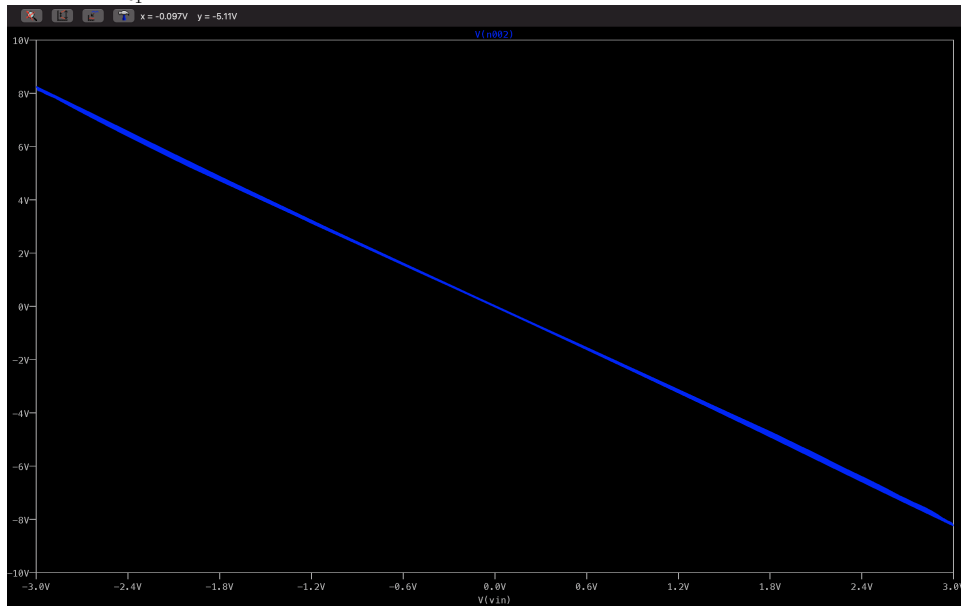
b.  $V_3 = V_2 = 0$

$$V_{out} = -\frac{V_{in}}{R_1} \times R_2$$



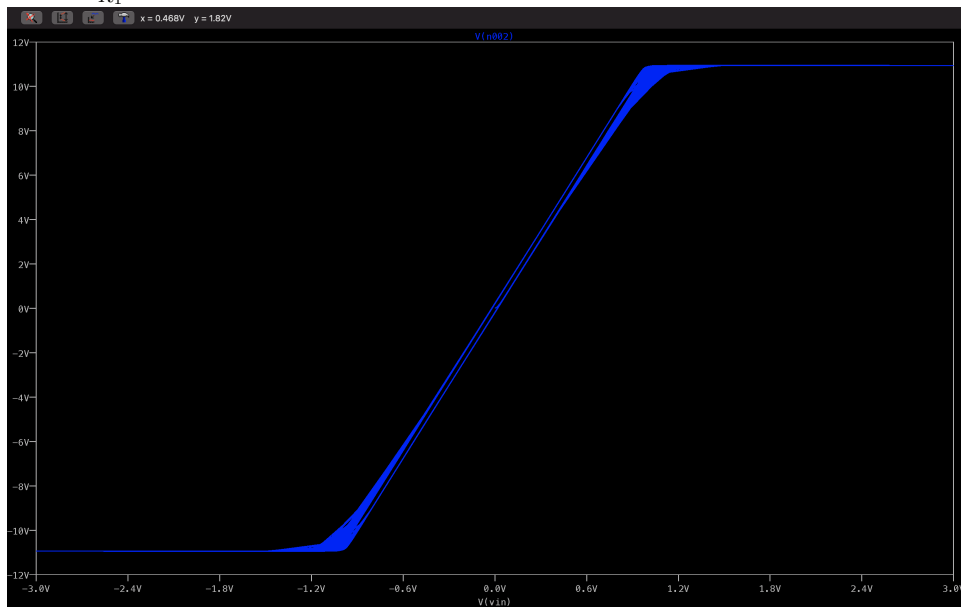c.  $V_3 = V_2 = V_{in}$

$$V_{out} = \frac{V_{in}}{R_1} \times R_2 + V_{in}$$




## 1.2 Question 2

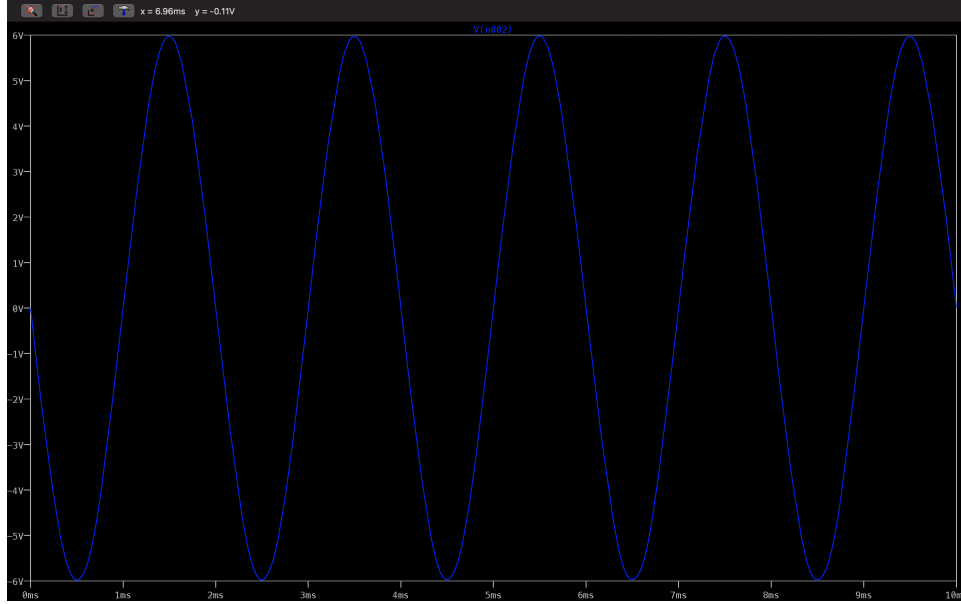a.  $V_3 = V_2 = 0$

$$\left( \frac{V_a(t)}{R_1} + \frac{V_b(t)}{R_2} \right) \times R_f$$


$= -(V_a(t) + V_b(t))$  So, this is an addition opamp.



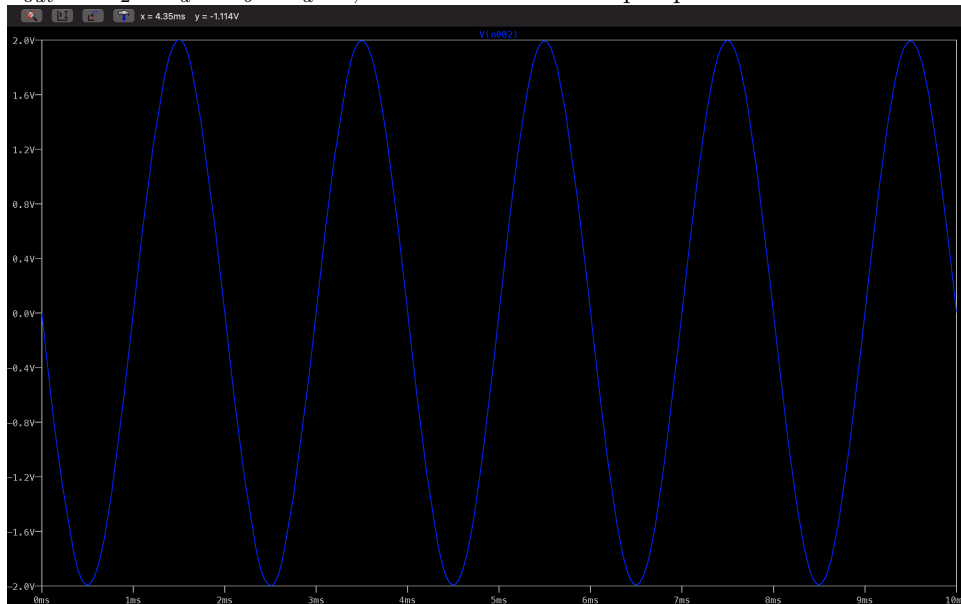b.  $V_3 = V_2 = \frac{V_b}{R_2 + R_4} \times R_4$

$$V_{out} = -\frac{V_a - V_2}{R_1} \times R_3 + V_2$$

$V_{out} = 2V_2 - V_a = V_b - V_a$  So, this is an extraction opamp.



c.  $V_3 = V_2 = \frac{V_i n - 2}{R_1 + R_2} \times R_2 + 2V$


$$V_{out} = \frac{V_2}{R_1} \times R_2 + V_2$$

$$V_{out} = \frac{33 \times V_{in} - 200}{100}$$

## 2 Experimental Work
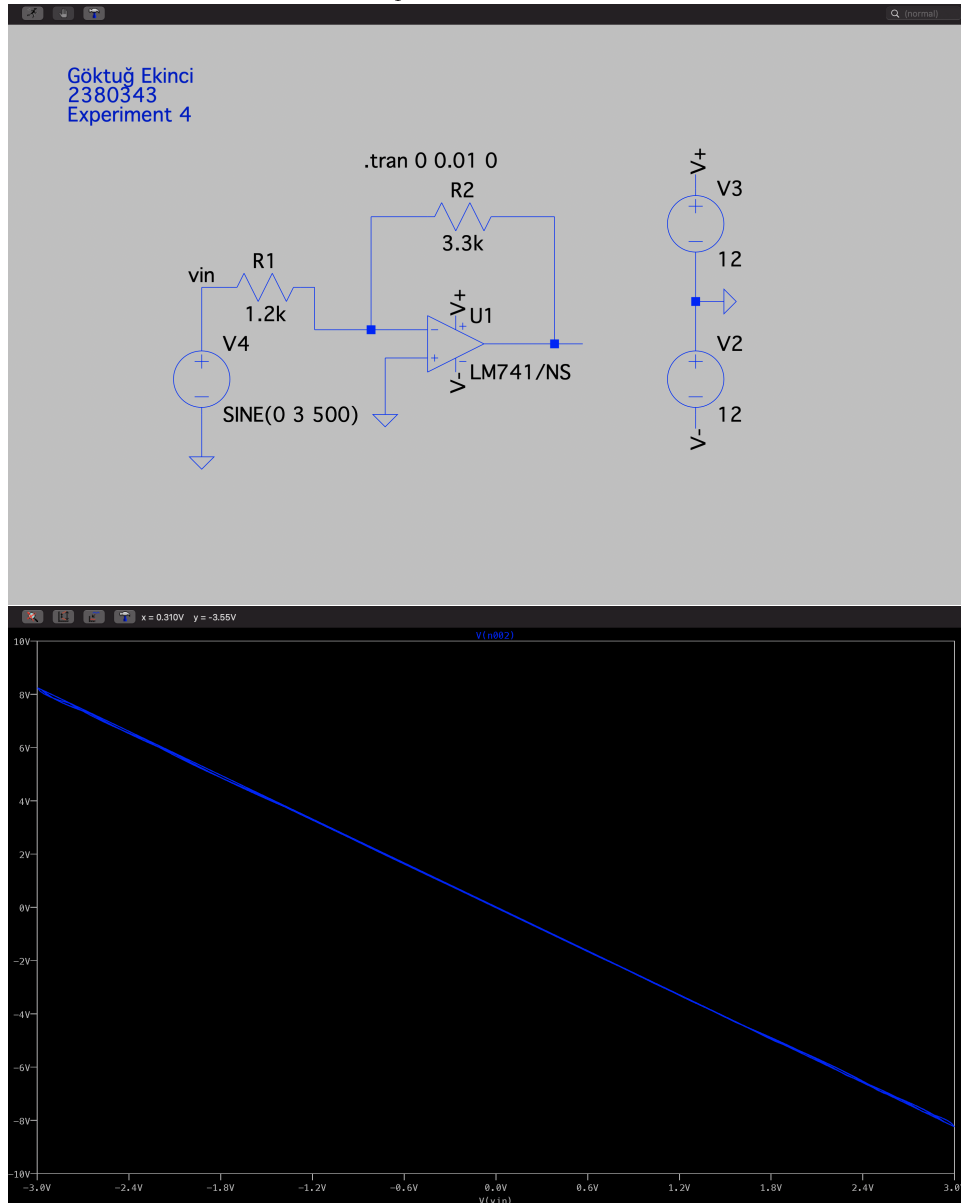
### 2.1 Figure 1&2


Set up the Figure 5 and adjusted voltage source to sinusoidal wave form, 500Hz and 3 for amplitude. Added a label right after  $V_{in}$ .  $V_{out} = -\frac{V_{in}}{R_1} \times R_2$



Experimental Gain:  $16/6 = 2.67$
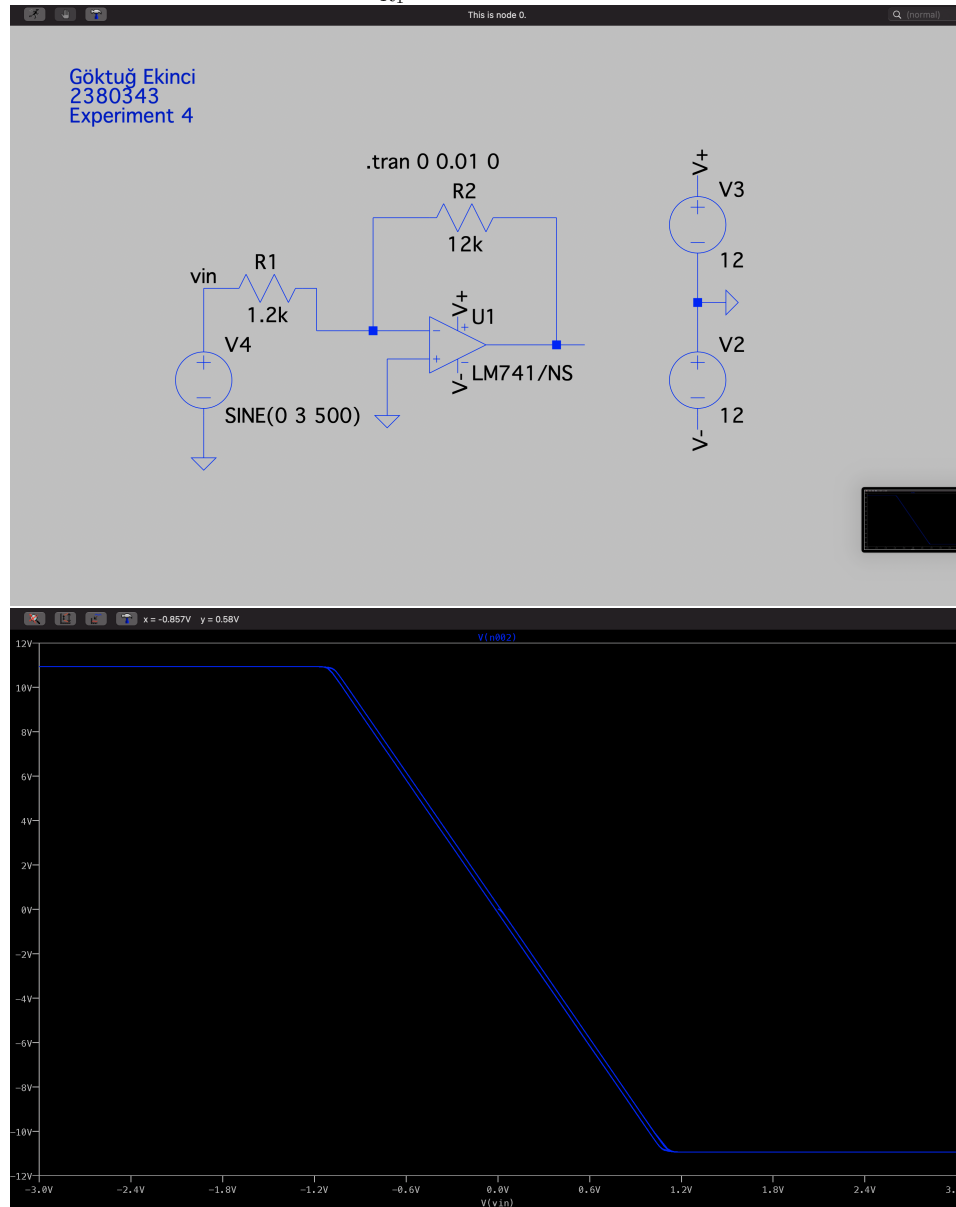
## 2.2 Figure 3&4


Set up the Figure 10 and adjusted voltage source to sinusodial wave form, 500Hz and 3 for amplitude. Added a label right after  $V_{in}. V_{out} = -\frac{V_{in}}{R_1} \times R_2$



Experimental gain except the saturation: -9.8
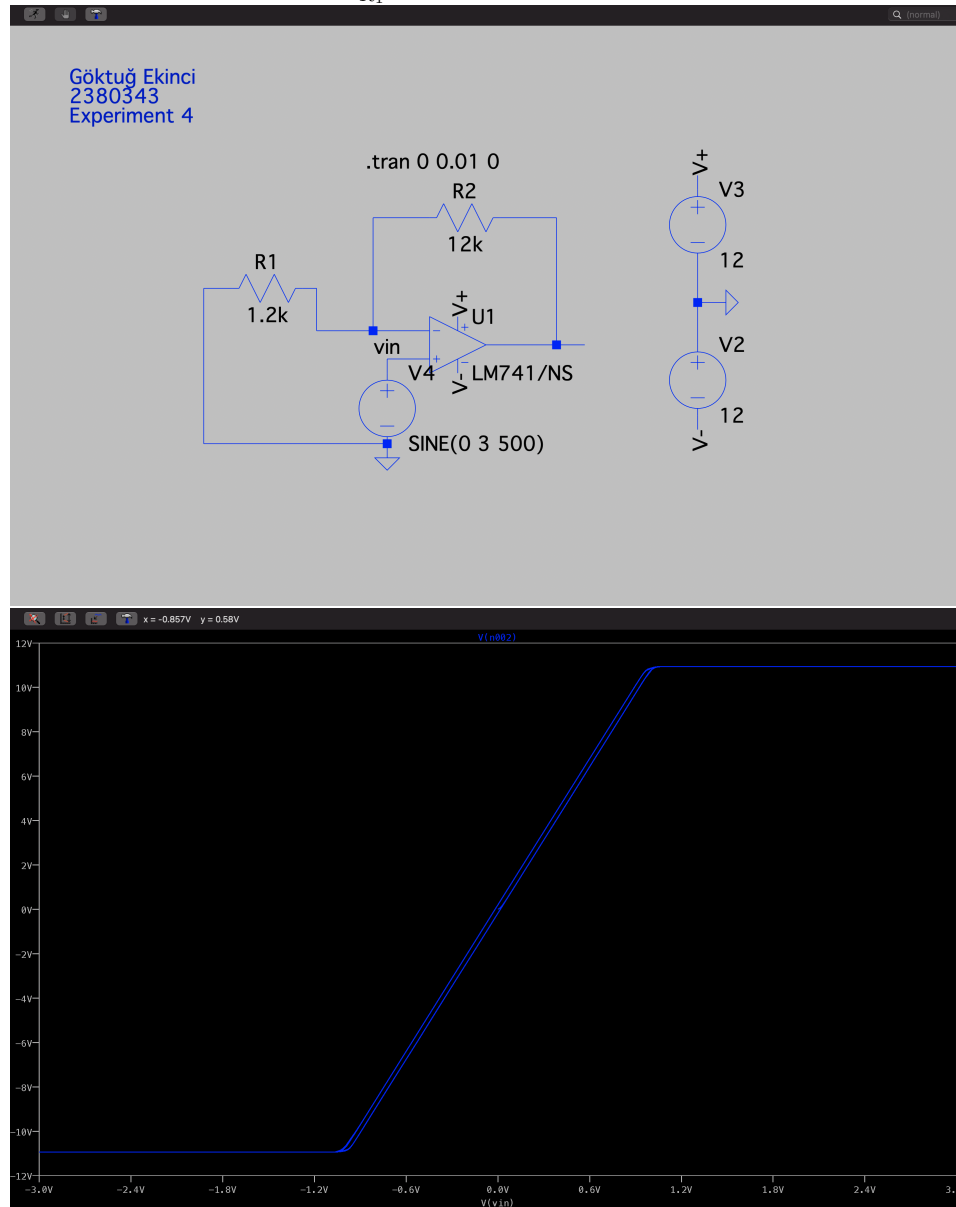
## 2.3 Figure 5&6


Set up the Figure 6 and adjusted voltage source to sinusoidal wave form, 500Hz and 3 for amplitude. Added a label right after  $V_{in} \cdot V_{out} = \frac{V_{in}}{R_1} \times R_2 + V_{in}$



Experimental gain except the saturation: 10.3

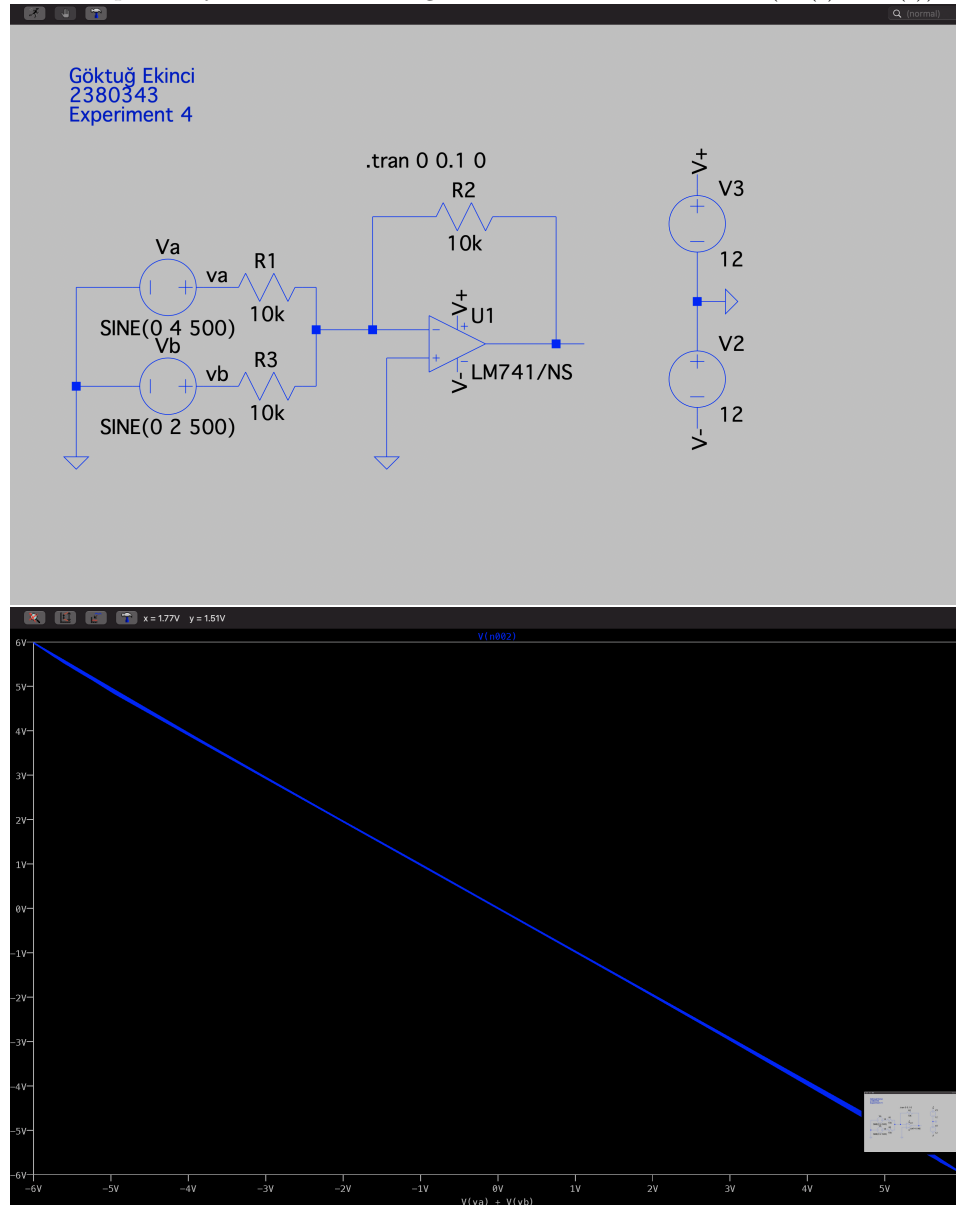
## 2.4 Figure 7&8

Set up the Figure 7 and adjusted voltage sources to sinusoidal wave form, 500Hz for both and 2,4 for amplitudes respectively. Added a label right after  $V_a$  and  $V_b$ .  $V_{out} = -(V_a(t) + V_b(t))$


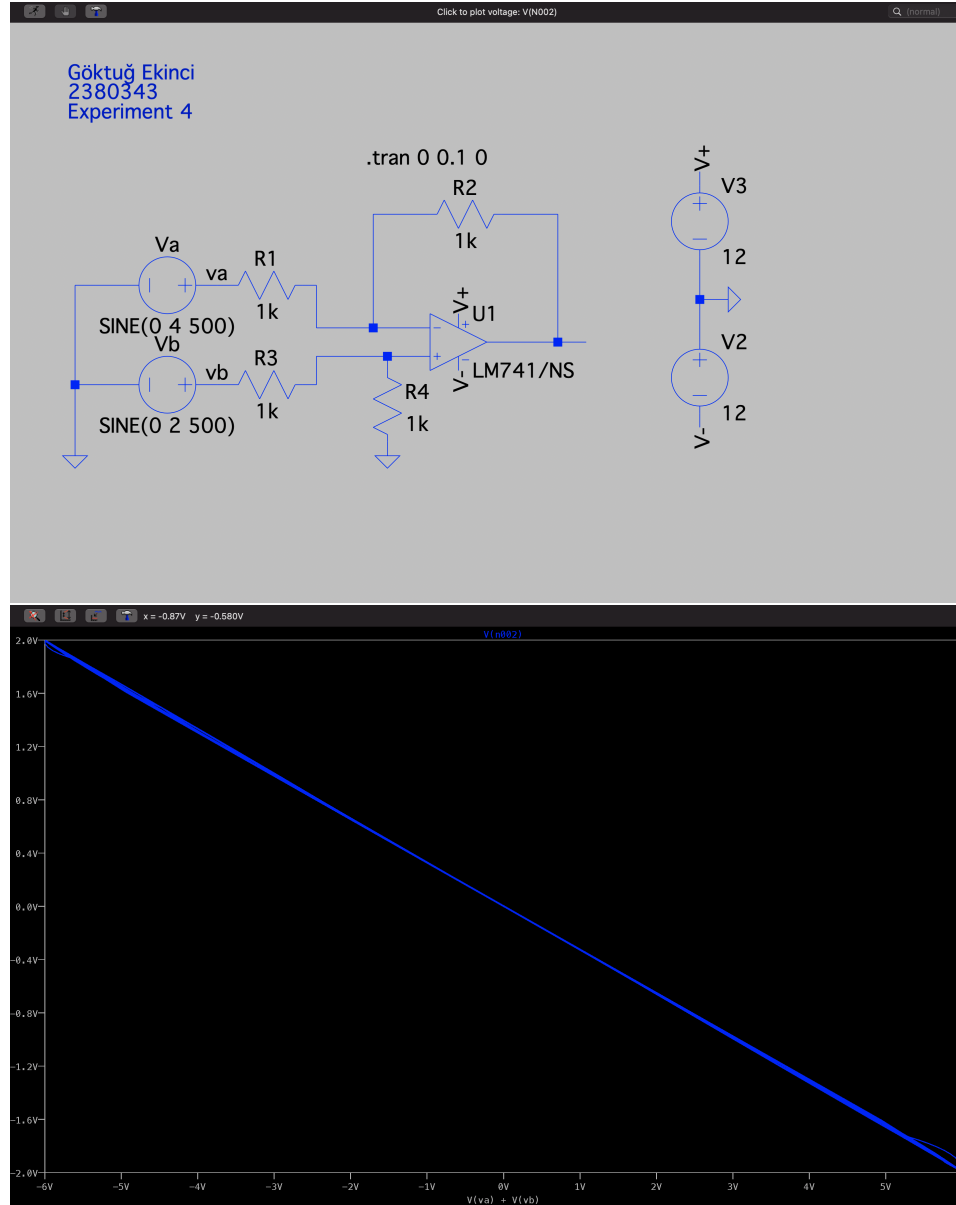
## 2.5 Figure 9&10

Set up the Figure 8 and adjusted voltage sources to sinusoidal wave form, 500Hz for both and 2,4 for amplitudes respectively. Added a label right after  $V_a$  and  $V_b$ .  $V_{out} = V_b(t) - V_a(t)$




Slopes are both  $-1 = V_{out}/V_{in}$ .


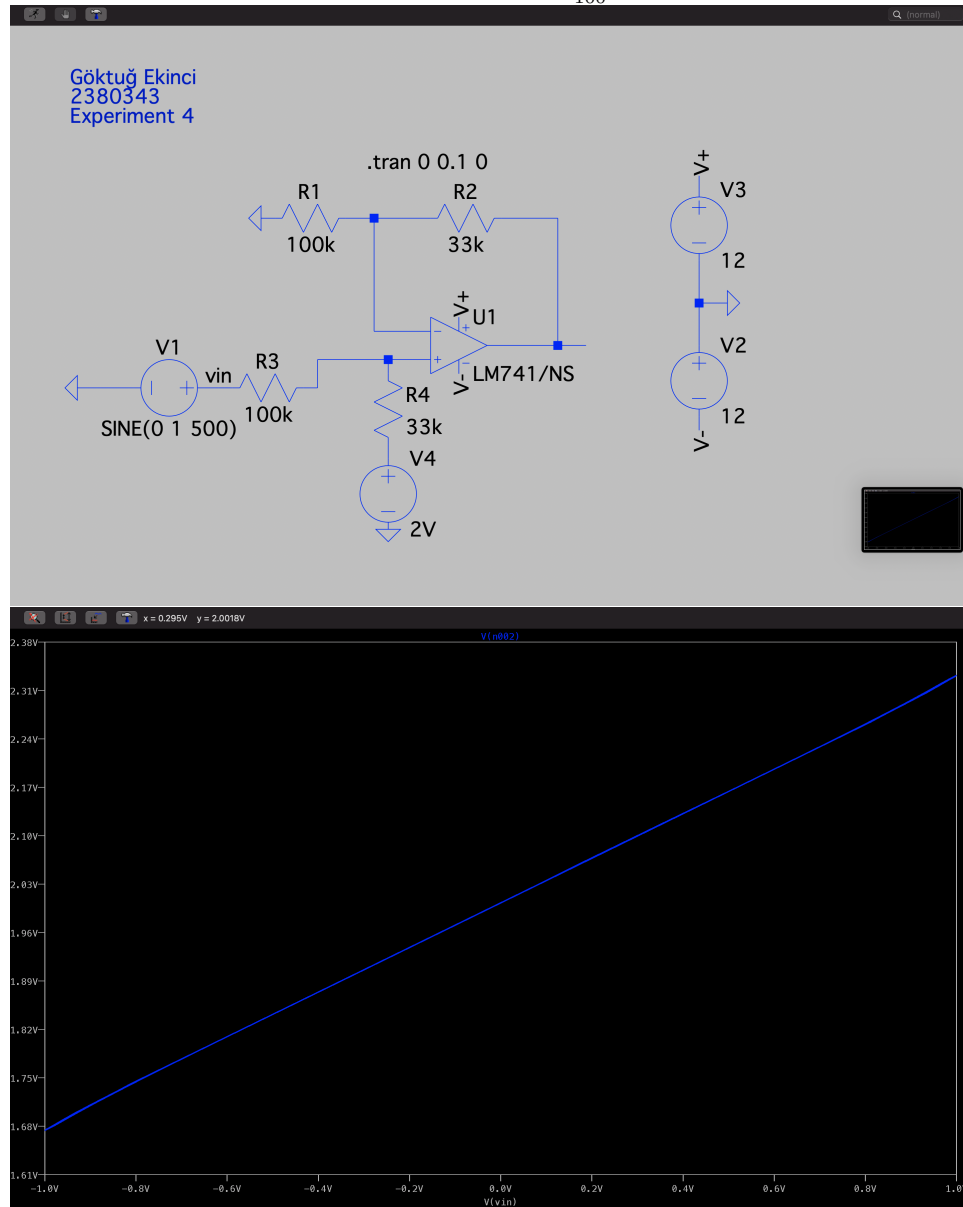
## 2.6 Figure 11&12

Set up the Figure 9 and adjusted voltage source to sinusoidal wave form, 500Hz and 1 for amplitude respectively. Added a label right after  $V_{in}$ .  $V_{out} = \frac{33 \times V_{in} - 200}{100}$



Slope:  $33/100$ .