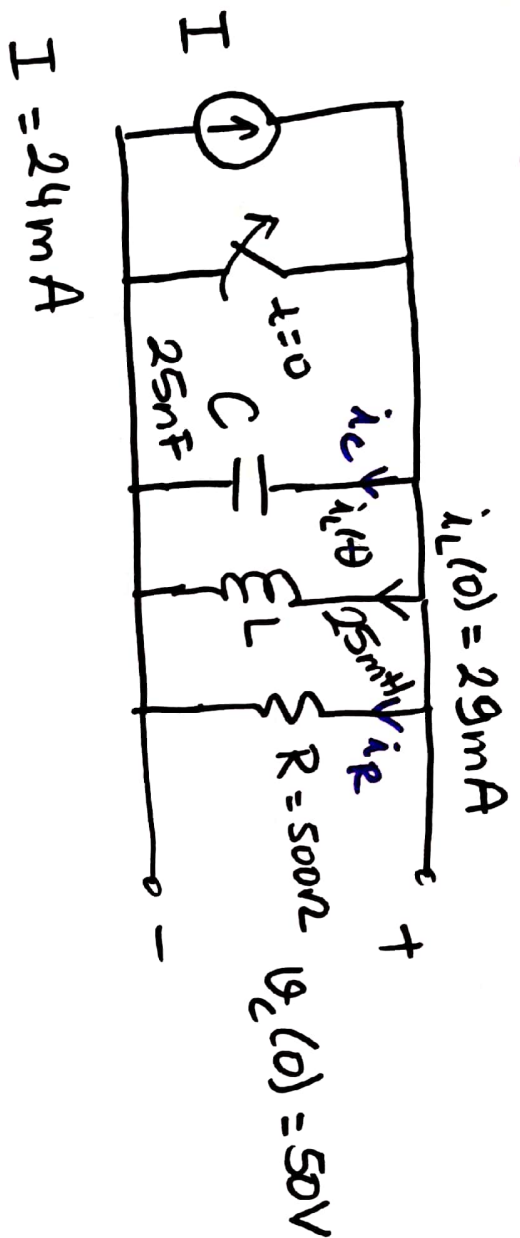


Parallel RLC forced response with non zero initial conditions



$$I = i_C + i_L + i_R$$

$$C \frac{dv_C}{dt} + i_L + \frac{v_C}{R} = I$$

$$v_C = v_L = L \frac{di_L}{dt} \quad \frac{dv_C}{dt} = L \frac{d^2 i_L}{dt^2}$$

$$CL \frac{d^2 i_L}{dt^2} + i_L + \frac{L}{R} \frac{di_L}{dt} = I$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 500 \times 25 \times 10^{-9}} = \frac{10^6}{25} = 4 \times 10^4 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{25 \times 10^{-3} \times 25 \times 10^{-9}}} = \frac{1}{25 \times 10^{-6}} = 4 \times 10^4 \text{ rad/s}$$

$$\frac{di_L}{dt}(0) = \frac{v_C(0)}{L}$$

Forced

$$i_L(t) = I_f$$

Steady-state constant value

$$+ I_n$$

natural response
Depending on α ,
 ω_0 one of the
3 solutions

There are two coefficient
to be determined by
using these initial
conditions.

$\alpha = \omega_0 \Rightarrow$ critically damped

$$i_L(t) = 24 \times 10^{-3} + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$


$$i_L(0) = 24 \times 10^{-3} + D_2 = 29 \text{ mA} = 29 \times 10^{-3} \text{ A} \Rightarrow D_2 = 5 \times 10^{-3} \text{ A}$$

$$\left. \frac{di_L}{dt} \right|_{t=0} = D_1 \left(\cancel{e^{-\alpha t}} + t \cancel{(-\alpha) e^{-\alpha t}} \right) + D_2 \underbrace{(-\alpha) e^{-\alpha t}}_1 = D_1 - \alpha D_2$$

$$D_1 - 4 \times 10^4 \times 5 \times 10^{-3} = \frac{V_c(0)}{L} = \frac{50}{25 \times 10^{-3}} \Rightarrow D_1 = 2200 \text{ A/s}$$

$$i_L(t) = 24 + 2.2 t e^{-4000t} + 5 e^{-4000t} \text{ mA}$$

Series RLC forced response

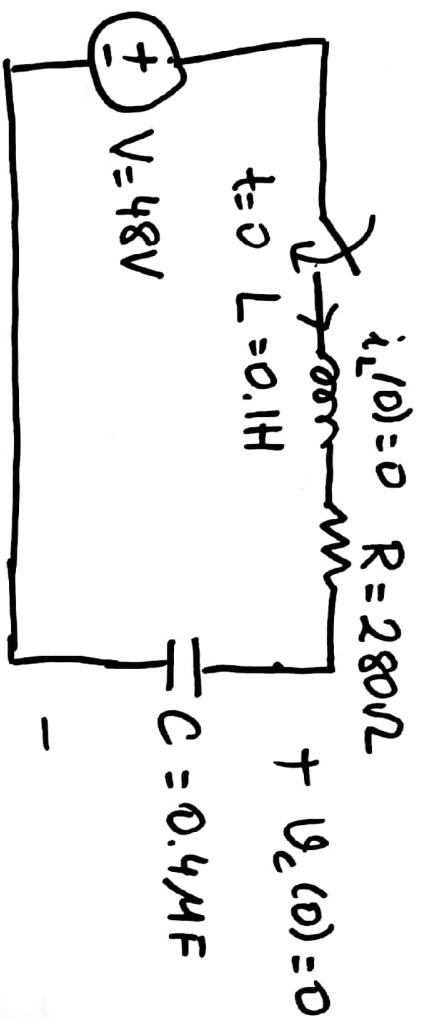

$$V = LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C$$

$$\alpha = \frac{R}{2L} = \frac{280}{2 \times 0.1} = 1400 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \times 0.4 \times 10^{-6}}} = 5000 \text{ rad/s}$$

$\omega_0 > \alpha \Rightarrow$ underdamped

$$V = v_L + v_R + v_C$$

$$V = L \frac{di_L}{dt} + i_L R + v_C$$

$$i_L = i_C = C \frac{dv_C}{dt}$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V}{LC}$$

$$v_C(t) = V_f + V_n \rightarrow \text{One of 3 solutions}$$

Steady-state final value

$$v_C(0) = \frac{dv_C(0)}{dt} = \frac{i_L(0)}{C}$$

$$v_c(t) = 48V + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$v_c(0) = 48 + B_1 = 0 \Rightarrow B_1 = -48V$$

$$= 4800$$

$$\frac{dv_c(0)}{dt} = \frac{i_L(0)}{C} = 0$$


$$\left. \frac{dv_c(t)}{dt} \right|_{t=0} = B_1 \left(\underbrace{-\alpha e^{-\alpha t}}_1 \cos \omega_d t \right) + B_2 \left(e^{-\alpha t} \left(-\alpha \sin \omega_d t + e^{\omega_d t} \cos \omega_d t \right) \right)$$

$$= -\alpha B_1 + \omega_d B_2 = 0$$

$$B_2 = \frac{1400(-48)}{4800} = -14V$$

$$v_c(t) = 48 + (-48) e^{-1400t} \cos 4800t + (-14) e^{-1400t} \sin 4800t$$

(4)

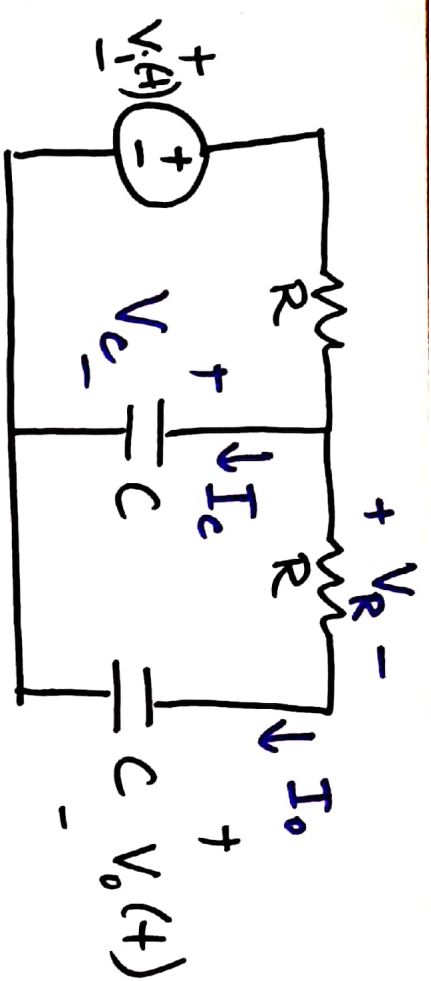

Find DE in terms of $V_o(t)$

$$-V_c + V_R + V_o = 0$$

$$V_c = R I_o + V_o = R C \frac{dV_o}{dt} + V_o$$

$$I_c = C \frac{dV_c}{dt} = R C^2 \frac{d^2 V_o}{dt^2} + C \frac{dV_o}{dt}$$

$$-V_i + R(I_c + I_o) + V_c = 0$$

$$R(RC^2 \frac{d^2 V_o}{dt^2} + C \frac{dV_o}{dt} + C \frac{dV_o}{dt}) + RC \frac{dV_o}{dt} + V_o = V_i$$

$$R^2 C^2 \frac{d^2 V_o}{dt^2} + 3RC \frac{dV_o}{dt} + V_o = V_i$$

$$\frac{d^2 V_o}{dt^2} + \frac{3}{RC} \frac{dV_o}{dt} + \frac{V_o}{R^2 C^2} = \frac{V_i}{R^2 C^2}$$

(5)